

CIS 240 – Computer Architecture Report

Below is a cohesive, integrated report that merges your existing content (on the complete adder and simplified computer architecture) with additional insights from your “new-circuits” directory. You can copy this as is or adapt headings/formatting to align with your lab requirements.

1. Introduction

This lab project explores the design and integration of a 4-bit adder into a simplified computer architecture. The system includes:

- **Carry-Lookahead Adder (CLA)-based ALU:** Performs addition and subtraction.
- **Register File:** Provides storage for operands and results.
- **Instruction Memory (program ROM) and Data Memory (SRAM):** Holds instructions and data.
- **Control Unit:** Decodes instructions and orchestrates data movement between components.

Objective: Demonstrate how the complete adder design fits into the overall computer architecture and verify correct functionality via a short program.

2. Complete Adder Implementation

2.1 Structure Overview

- The system uses a **4-bit CLA Adder** within the ALU, enabling single-cycle addition and subtraction.

- Internally, the CLA uses half adders and full adders, optimized to reduce carry propagation delay.
- When the **AddSub** control signal is asserted:
 - **AddSub=0**: Perform **addition**.
 - **AddSub=1**: Perform **subtraction** (by inverting one operand and adding a carry of 1).

2.2 Half Adder and Full Adder

1. Half Adder

- Takes two single bits (A, B).
- Produces a **sum** and a **carry** bit.

2. Full Adder

- Extends the half-adder with an incoming carry.
- Produces a final sum and an outgoing carry.

2.3 Carry-Lookahead Adder (CLA) Concept

A CLA pre-computes carry bits in parallel using **Generate (G)** and **Propagate (P)** signals:

- $G_i = A_i \cdot B_i$
- $P_i = A_i \oplus B_i$
- $C_{i+1} = G_i + (P_i \cdot C_i)$

For a 4-bit block, this parallel carry calculation greatly speeds up addition and subtraction compared to ripple-carry designs.

2.4 Integration into the ALU

- **ALU Operation:**
 - Reads two registers (operands) from the register file.
 - Applies CLA-based addition or subtraction.
 - Writes the result back to the destination register.

- **Outputs:**

- Sum[3:0]: 4-bit arithmetic result.
 - Cout: Carry-out for detecting overflow or carry.
-

3. The Computer Architecture

3.1 Major Components

1. Instruction Memory

- Stores 8-bit instructions.
- Program Counter (PC) increments to fetch each instruction in sequence.

2. Register File

- Holds multiple 4-bit registers (e.g., R0, R1, R2, R3).
- Supports two reads (operands) and one write (result) per cycle.

3. Data Memory

- Four 4-bit memory locations (addresses 0–3).
- Used by LOAD and STORE instructions.

4. ALU (with CLA)

- Performs 4-bit addition or subtraction.
- Receives operands from the register file.
- Produces a 4-bit result.

5. Control Unit

- Decodes the 8-bit instruction.
- Manages control signals (AddSub, WrMem, WrReg, etc.).

3.2 Instruction Set Architecture

All instructions are 8 bits wide, following this format:

[OPCODE (2 bits)] [Register/Operand fields (5 bits)] [Unused (1 bit)]

We define four primary instructions:

1. **ADD (00)**

- Format: 00 dest[2:0] X src[1:0]
- Action: dest = dest + src

2. **SUB (01)**

- Format: 01 dest[2:0] X src[1:0]
- Action: dest = dest - src

3. **STORE (10)**

- Format: 10 reg[2:0] X addr[1:0]
- Action: Write contents of reg to DataMem[addr].

4. **LOAD (11)**

- Format: 11 reg[2:0] X addr[1:0]
- Action: Read from DataMem[addr] into reg.

Note:

- dest/reg is a 3-bit register specifier (e.g., R0=000, R1=001, R2=010, R3=011).
- src can also be a register specifier.
- addr[1:0] is a 2-bit memory address (0–3).

3.3 Sample Program

```
LOAD  R0, 0    ; (11 000 X 00) -> Load DataMem[0] into R0
LOAD  R1, 1    ; (11 001 X 01) -> Load DataMem[1] into R1
ADD   R3, R1   ; (00 011 X 01) -> R3 = R3 + R1 (initially R3 = 0)
STORE R3, 3    ; (10 011 X 11) -> Store R3 into DataMem[3]
```

1. LOAD R0,0: Transfers data from DataMem[0] into R0.
 2. LOAD R1,1: Transfers data from DataMem[1] into R1.
 3. ADD R3,R1: Performs addition with the ALU's CLA.
 4. STORE R3,3: Writes the result to DataMem[3].
-

4. Implementation Details

4.1 Data Path

1. Instruction Fetch

- PC -> Instruction Memory.
- The instruction is latched into the Instruction Register.

2. Instruction Decode

- Control Unit parses the 8-bit instruction.
- Determines if it's an ALU or memory operation.

3. Execution

- ADD/SUB: ALU reads specified registers, performs arithmetic.
- LOAD/STORE: The address lines connect to Data Memory.

4. Write-Back

- ALU result or loaded data is written to the destination register.

4.2 Control Flow

- **Single-cycle design:** fetch, decode, execute, and write-back occur in one clock cycle (simplified model).
 - **Control signals** (`WrMem`, `WrReg`, `AddSub`, etc.) are enabled/disabled by the Control Unit.
-

5. Testing and Verification

5.1 Adder Testing

- **Component-Level:** Verify half-adder and full-adder truth tables.
- **Integration:** Confirm correct carry output across multiple bits.

5.2 System-Level Testing

- **Simulation:** Use test benches that run sequences of instructions, checking register contents and memory updates.
- **Edge Cases:** Test memory boundary addresses (0 and 3) and verify overflow handling.

5.3 Example Test Bench Requirements

- **Timing:** Setup and hold times of $\sim 1\text{ns}$ each, max propagation delay $\sim 10\text{ns}$.
 - **Worst-Case Inputs:** e.g., `0xF + 0xF` to test maximum carry generation.
 - **Memory:** Confirm correct data retrieval and storage timing.
-

6. Performance Characteristics

- **Single-Cycle Operation:** One instruction per clock cycle for the simplified design.
- **CLA Adder Delay:** Logarithmic in bit-width (4 bits, effectively minimal here).

- **Memory Latency:** Minimal for in-lab SRAM with synchronous R/W.
-

7. Incorporating “new-circuits” Directory Insights

In your **new-circuits** directory, you have various `.asc` (LTSpice schematic) and `.asy` (symbol) files indicating a modular approach. These circuits align with the architecture described above:

1. Registers and Memory

- **RegisterBank.asc:** Implements the multi-register file.
- **DataMem.asc:** Provides 4-bit memory locations.
- **Integration:** The register bank and data memory directly interface with the ALU and control signals.

2. Logic Gates and Multiplexers

- **MUX4.asc:** 4-to-1 multiplexer essential for routing data within the CPU.
- **NAND.asc, NOR.asc:** Fundamental logic gates used in sub-circuits.

3. Control and Processing

- **ALU.asc:** Your top-level ALU design, integrating the 4-bit CLA.
- **PC.asc:** A simple program counter that increments to fetch instructions sequentially.

4. Test Benches

- Files like **RegFileTest.asc** and **MUXtest.asc** contain simulation directives (`.tran`, etc.) to verify each module’s functionality.

Best Practices Observed

- **Clear SYMATTR usage:** Each schematic file clearly labels components with instance names and values.
- **Subcircuit approach:** Modular design for easier debugging, reusability, and clarity.
- **Simulation directives:** `.tran` statements demonstrate timing checks and functional validation.

7.1 Updating Documentation

- **Include Descriptions:** Document each `.asc` file's purpose in your final report or lab notes (e.g., `RegisterBank.asc` → holds R0–R3 registers).
 - **Explain Integration:** Show how data travels from `RegisterBank.asc` → `ALU.asc` → `DataMem.asc` under control signals.
 - **Highlight Testing:** Summarize how `RegFileTest.asc` and `MUXtest.asc` confirm correct read/write operations and multiplexing logic.
-

8. Conclusion

By incorporating a **4-bit Carry-Lookahead Adder** within the ALU, this design supports efficient addition and subtraction. The instruction set (ADD, SUB, LOAD, STORE) handles fundamental operations, and a single-cycle approach keeps control logic straightforward. Testing confirms each subsystem (ALU, register file, memory, etc.) works correctly, as demonstrated by the example program and the **new-circuits** test benches.

Version: 1.2

Last Updated: [Insert Date]

Status:

- Added complete adder design notes, instruction set details, and “new-circuits” references.
 - Updated with sample program, test methodology, and recommended next steps.
-

Suggested Next Steps

1. **Extend the Instruction Set:** Add branching (JMP, BEQ) for more complex control flow.
2. **Expand Memory:** Increase data memory locations beyond the current 4.

3. **Pipeline the Design:** Move from a single-cycle architecture to multi-stage pipelining for higher clock speeds.

Note: Adjust register numbering, opcodes, or instruction widths to match your actual class deliverables if they differ from the examples above.

Final Note & Further Refinements

- For more advanced simulation, consider adding **timing constraints** for each component in LTSpice or a Verilog/VHDL environment.
- If you integrate the **register bank** and **control logic** into a single schematic or an HDL project, ensure you maintain a **consistent naming convention**.

Solution Endpoint:

You now have a consolidated report reflecting both the **complete adder** and the **simplified computer architecture** details—plus the **new-circuits** directory insights. Feel free to adapt any section headings, add diagrams, or refine your test benches as needed. Let me know if you need any additional adjustments or clarification!